

Name: \_\_\_\_\_

Section: \_\_\_\_\_

# Measuring Electricity

## Before You Begin

### GLOBAL CONTEXT (Orientation in Space & Time)



q1 Choose a predicted near-future invention and explain how it would have an impact on human development.

### KEY CONCEPT (Development)



q2 Our statement of inquiry revolves around the concept of *development*, particularly *human development*. How would you define human development? Give some specific examples.

### RELATED CONCEPT (Invention)



q3 We are examining the invention of electrical circuits as a *turning point* in history. What other inventions do you think resulted in an historical turning point?

q4 Do you believe that any invention in history represented a set-back to human development? Why or why not?



## Technical Background

This lesson will be primarily concerned with the way we measure electricity within our circuits, and how we can select appropriate components based on the amount of electricity supplied and/or required.

### Voltage

Voltage, measured in *volts* (**V**), is a *potential* difference between a positively and negatively charged part of a circuit. A common example illustrating the concept of voltage that of a water tank or tower.

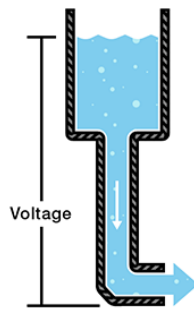


Image courtesy sparkfun.com.

In this illustration, voltage can be seen as equivalent to the *water pressure* coming out of the hose at the bottom of the system. Factors such as the height and size of the tank can have an impact on how much pressure is available. This is the *potential energy* concept. While batteries and other sources of electricity provide power in different ways, the analogy is still useful for understanding what voltage contributes to an electrical circuit.

### Voltage Drop / Forward Voltage

*Voltage Drop* or *Forward Voltage* is the amount of voltage required to power a load or other component in an electrical circuit.

#### Kirchhoff's Voltage Law

*Kirchhoff's Voltage Law* (or *Kirchhoff's Second Law*) essentially states that sum of all voltage drops in a closed electrical circuit, such as the simple circuits we built in the previous lesson, will be equal to the voltage of the source.

### Current

Current, measured in *amperes* (**A**), is the *flow* of electricity within a circuit. You can think of current as the *speed* at which electricity flows.

#### ATL SKILL (Communication Skills)

...make inferences and draw conclusions...

**q5** Considering the water tank example given above for voltage, what changes to the system would have an impact on the flow of water out of it?

## Forward Current

Similar to forward voltage, forward current is the amount of current required by a load or component to work properly. As we will see later, the *maximum* forward current is often supplied by device manufacturers, which indicates how much current the device or component can handle before becoming damaged. This value will have a significant impact on how we design our circuits.

**Note:** One ampere (**1A**) represents a significant amount of current for our simple components. Because of this, we will often discuss maximum forward current in terms of milliamperes (**mA**), or “milliamps”. One milliamp represents  $\frac{1}{1000}$  of an ampere.

**Example:** A typical maximum forward current we will see is **20mA**. This represents  $\frac{20}{1000}$ , or **0.02A**.

## Resistance

Resistance, measured in Ohms ( $\Omega$ ), is a property of different materials to resist the flow of electricity within a circuit.

## Conductor v. Insulator

Materials can be divided into two broad categories: conductors and insulators. A *conductor* offers little resistance to the flow of electricity, while an *insulator* provides significant resistance. For example, copper wire is a conductor while most plastics are insulators.

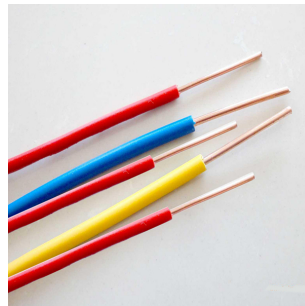



Image courtesy of sparkfun.com.

The above image shows a copper wire that has been stripped of some of its plastic sheath insulation.

ATL SKILL (Communication Skills) 
...make inferences and draw conclusions...
<b>q6</b> Why do conductive wires often get wrapped in an insulating material, like in the image above?
<b>q7</b> Many of the components we are going to be using are made using a <i>semiconductor</i> material. How do you think semiconductors compare to conductors and insulators?

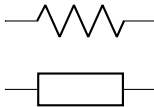

## Ohm's Law

### Ohm's Law

Ohm's Law provides us with a very simple formula linking voltage (**V**), current (**I**), and resistance (**R**):

$$V = IR \quad \text{OR} \quad I = \frac{V}{R} \quad \text{OR} \quad R = \frac{V}{I}$$

## The Resistor

Name	Description	Symbol	Example
<b>Resistor</b>	<p>A <i>resistor</i> is an electronic component specifically designed to reduce the current flow in a circuit.</p> <p>The <i>resistance</i> offered by each resistor is measured in Ohms (<math>\Omega</math>).</p>		

The type of resistor we will be using are labeled using coloured bands to denote their resistance. You have a copy of the following image in your electronics kits:

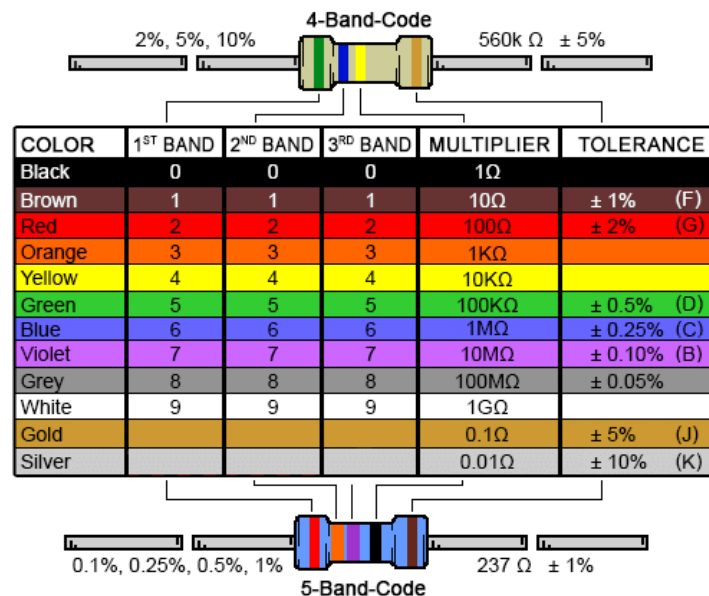


Image courtesy digikey.com.

### ATL SKILL (Communication Skills)

...use and interpret a range of discipline-specific terms and symbols...

**Q8** Throughout this course, we will be using a variety of different resistors. The following resistance value resistors are quite common: 220 $\Omega$ , 1k $\Omega$ , 10k $\Omega$ . These are available in your electronics kit. Determine whether your resistors are 4— or 5—band and identify the correct colour bands for each required value. You can safely ignore the “tolerance” band for now.

**220  $\Omega$**

**1 k $\Omega$**

**10 k $\Omega$**

## Developing Technical Skills

### Circuit #4: Higher Voltages


This circuit uses a 9-volt battery to examine how voltage impacts the performance of circuit components. Note that you might need to hold the 9-volt battery in place. If this is proving difficult, team up with a partner who can help you operate the circuit with the battery properly positioned.

#### You Will Need:

- (1) 9V Battery
- (1) LED
- (1) Pushbutton
- (1) Roll of Copper Tape
- (1) Roll of Cellophane Tape
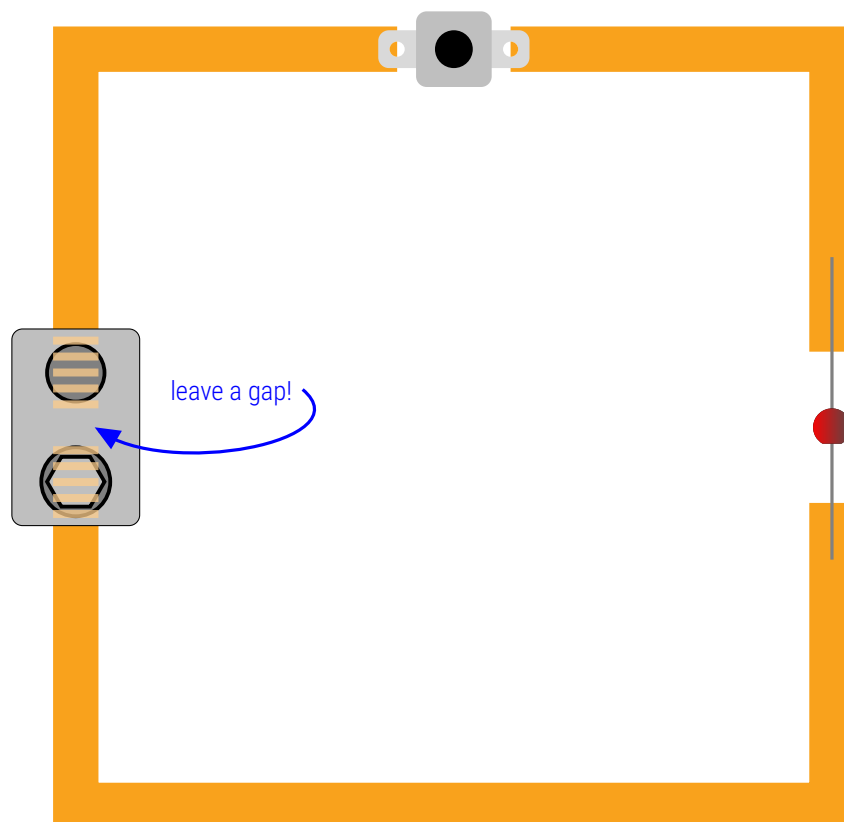
#### Directions

Create the following paper circuit. Note the position of the different sized terminals on the 9V battery.



#### ATL SKILL (Communication Skills)


...make inferences and draw conclusions...

**Q9** What happens when you power the above circuit? Did you expect that to happen? Attempt an explanation based on the technical details discussed earlier, particularly the relationship between voltage and current.
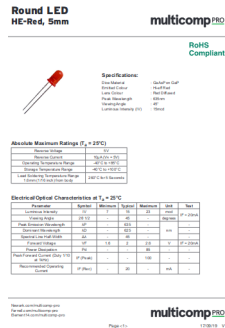
## Examining Datasheets

A *datasheet* is a technical document listing important details about each specific component we will use in our circuits. While these had traditionally been packaged with purchased items, most of the time they are now just a quick Google search away.

The following two images show first an overview of a datasheet for one of the red LEDs we have been using, then the specific area of the datasheet we will be interested in for this lesson.



An overview of an entire datasheet, courtesy element14.com.

### Electrical/Optical Characteristics at $T_a = 25^\circ\text{C}$

Parameter	Symbol	Minimum	Typical	Maximum	Unit	Test
Luminous Intensity	IV	7	15	23	mcd	IF = 20mA
Viewing Angle	2 $\theta$ 1/2	-	45	-	degrees	
Peak Emission Wavelength	$\lambda_P$	-	635	-	nm	-
Dominant Wavelength	$\lambda_D$	-	625	-		-
Spectral Line Half-Width	$\Delta\lambda$	-	45	-	-	-
Forward Voltage	VF	1.6	2	2.6	V	IF = 20mA
Power Dissipation	Pd	-	-	85	-	-
Peak Forward Current (Duty 1/10 at 1kHz)	IF (Peak)	-	-	100	-	-
Recommended Operating Current	IF (Rec)	-	20	-	mA	-

A zoom in on the "Electrical Characteristics" portion of the datasheet, with required details highlighted.

### ATL SKILL (Communication Skills)



...use and interpret a range of discipline-specific terms and symbols...

**q10** Using the information in the data sheet above, describe how *Kirchhoff's Voltage Law* explains why your two LED circuit from Lesson #1 did not function as intended.

**q11** Later this unit, we will be using a "BC547B Transistor". Find a datasheet for this component online and determine the current and voltage associated with "Small Signal Current Gain" ( $h_{fe}$ ).

## Circuit #5: Using Resistors


The following circuit solves the problem experienced in Circuit #4 by introducing a *resistor*. This will lower the current passing through the LED to below its maximum forward current rating (20 mA).

### You Will Need:

- (1) 9V Battery
- (1) LED
- (1) Pushbutton
- (1) Resistor (Yellow-Violet-Brown)
- (1) Roll of Copper Tape
- (1) Roll of Cellophane Tape
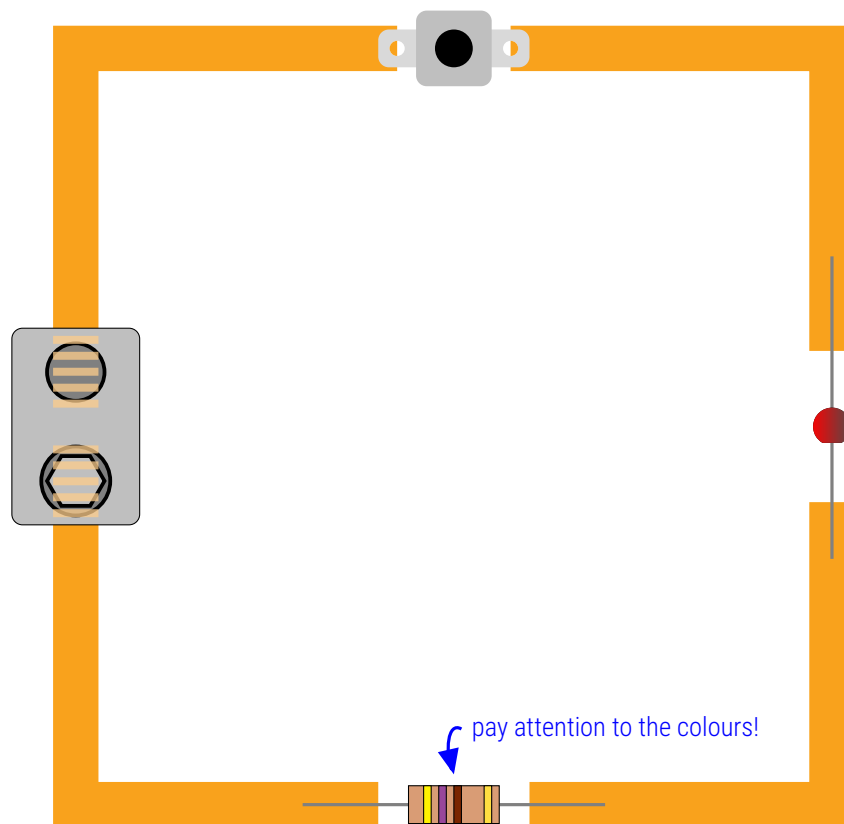
### Directions:

Create the following paper circuit. Note that unlike the LED, a resistor is *bidirection*; it does not need to be placed in any particular way.



#### ATL SKILL (Communication Skills)


...use and interpret a range of discipline-specific terms and symbols...

q12 What is the value of the resistor used in this circuit? Use your resistor colour band chart as reference.

## Finding the Perfect Resistor


The following process shows how we can determine what the appropriate resistor is for our simple circuits.

### Step 1:

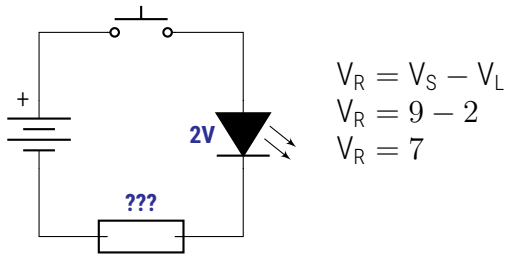


Determine the voltage drop across the resistor by using *Kirchoff's Voltage Law*. Remember: the total of the forward voltages across all components should be equal to the source voltage. The LED's voltage comes from its datasheet.

### Step 2:

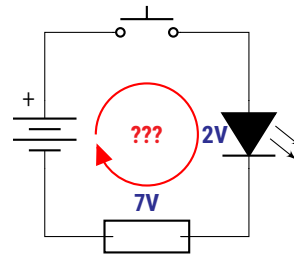


Determine the *desired* current. This is the maximum forward current from the LEDs datasheet (20 mA or 0.02A).

### Step 3:

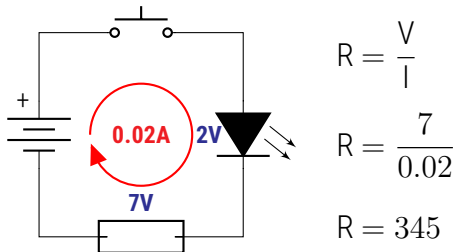

Apply *Ohm's Law* to calculate the resistance required across the resistor in the circuit.

### Step 4:

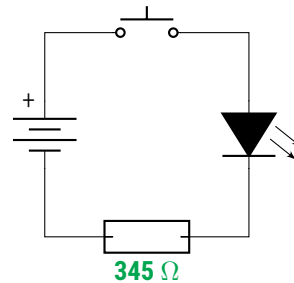

Typical circuit diagrams will include the resistor value as a label on each resistor.

#### ATL SKILL (Communication Skills)

...make inferences and draw conclusions...

q13 Why do you think we don't assign a forward voltage to the push button in our circuits?

q14 Despite the appropriate resistor is calculated as having a value of 345Ω, this is *not* the resistor we used in Circuit #5. Why do you think we chose a larger valued resistor for this circuit?



**FORMATIVE ASSESSMENT**



**Q15** Determine the correct resistor value for a simple circuit containing (2) LEDs.

**Q16** Draw the circuit diagram containing (2) LEDs and an appropriately sized resistor.

**Q17** Create a paper circuit version of your circuit diagram.

**Q18** What size resistor did you actually use for your circuit? Why did you choose this value?



## Reflections

### ATL SKILL (Communication Skills)



...make inferences and draw conclusions...

**Q19** What steps could you take to verify the inferences and conclusions you are making are accurate?

...use and interpret a range of discipline-specific terms and symbols...

**Q20** Adding additional information to a diagram is called *annotation*. Under what circumstances is it necessary to annotate a diagram, even if you can assume the special symbols are understood by all viewers?

**Q21** What aspect of this lesson was the most challenging for you? How did you overcome that challenge?

**Q22** Select the option which best reflects how confident you are in applying what you have learend in this lesson.



**Q23** What additional questions do you still have about this lesson's content?